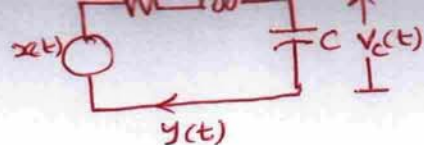


Applying KVL

$$x(t) - Ry(t) - L \frac{dy(t)}{dt} - V_c(t) = 0$$



$V_c(t)$  = Voltage across the capacitor

$$y(t) = C \frac{dV_c(t)}{dt}$$

$$\therefore V_c(t) = \frac{1}{C} \int_{-\infty}^t y(t) dt$$

$$\therefore x(t) - Ry(t) - L \frac{dy(t)}{dt} - \frac{1}{C} \int_{-\infty}^t y(t) dt = 0$$

Differentiating w.r. to  $t$ .

$$\frac{dx(t)}{dt} - R \frac{dy(t)}{dt} - L \frac{d^2y(t)}{dt^2} - \frac{1}{C} y(t) = 0$$

or

$$L \frac{d^2y(t)}{dt^2} + R \frac{dy(t)}{dt} + \frac{1}{C} y(t) = \frac{dx(t)}{dt}$$

Now  $R=2\Omega$   $L=C=1$

$$\therefore \frac{d^2y(t)}{dt^2} + 2 \frac{dy(t)}{dt} + y(t) = \frac{dx(t)}{dt}$$

Homogeneous solution is

$$\frac{d^2y(t)}{dt^2} + 2 \frac{dy(t)}{dt} + y(t) = 0$$

$$N=2$$

its solution is

$$y^h(t) = \sum_{i=1}^N C_i e^{\gamma_i t} = C_1 e^{\gamma_1 t} + C_2 e^{\gamma_2 t}$$

its characteristic equation is

$$\sum_{k=0}^{N=2} a_k \gamma^k = 0$$

$$a_0 \gamma^0 + a_1 \gamma^1 + a_2 \gamma^2 = 0$$

$$1 + 2\gamma + \gamma^2 = 0$$

$$\therefore (\gamma+1)^2 = 0$$

$$\therefore \gamma = -1, -1 \text{ (equal roots)}$$

$$\therefore y^h(t) = C_1 e^{-t} + C_2 t e^{-t}$$